

B.Tech III Year I Semester (R13) Supplementary Examinations November/December 2017

DIGITAL IC APPLICATIONS
(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- What are the advantages and disadvantages of CMOS technology?
 - List out the characteristics of ECL.
 - What are the data types available in VHDL?
 - What is binding?
 - Write a VHDL program for 2×4 decoder.
 - Write a VHDL program for 1×4 demultiplexer.
 - What is structural style of modeling?
 - Convert a D flip-flop into T flip-flop.
 - Distinguish between SRAM and ROM.
 - List out the applications of RAM.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) With reference to the dynamic behavior of CMOS explain about speed and power dissipation of CMOS circuits.
(b) Design CMOS transistor circuit for 3-input AND gate. With the help of function tables explain the operation of the circuit diagram.

OR

- 3 (a) Draw the circuit diagram of basic TTL NAND gate and explain the three parts with the help of functional operation.
(b) Explain the following terms with reference to TTL circuit:
(i) Logic levels. (ii) DC noise margin. (iii) High state fan-out.

UNIT – II


- 4 (a) Explain about dataflow design elements of VHDL.
(b) Explain the difference in program structure of VHDL and any other procedural language. Give an example.

OR

- 5 (a) Give the syntax and structure of a package in VHDL.
(b) Write a process based VHDL program for the prime-number detector of 4-bit input and explain the flow using logic circuit.

UNIT – III

 - 6 Obtain logical expression for the logic circuit shown and build the function with 8 to 1 (74x151) multiplexer. Assume BCD are select lines of 74x151.



OR

- 7 Design a 4x4 combinational multiplier and write the VHDL program in data flow model.

Contd. in page 2

UNIT – IV

- 8 (a) Draw the logic diagram of IC 74180 parity generator checker and explain its operation with the help of a truth table.
(b) With neat, sketch explain Barrel shifter.

OR

- 9 (a) Explain how a JK-flip-flop can be constructed using a T-flip-flop.
(b) Give a VHDL code for a 4-bit up counter with enable and clear inputs.

UNIT – V

- 10 Write short notes on the following:
(a) Two dimensional decoding.
(b) Read / write operation of DRAM.

OR

- 11 Determine the ROM size needed to realize the logic function performed by 74x153 and 74x139.
